

Physics Cup – TalTech 2019 – Problem 4. March 24, 2019

Consider an infinite square grid of resistors. Let us introduce coordinates x and y so that all the nodes are at integer coordinates (n, m) , with $n, m \in \mathbb{Z}$. For this grid of resistors, all the horizontal resistors, i.e. the resistors between node pairs $[(n, m), (n + 1, m)]$, have the same resistance R ; all the vertical resistors, i.e. the resistors between node pairs $[(n, m), (n, m + 1)]$ have the same resistance r . It appears that for such a grid, the effective resistance R_{nn} between the nodes $(0, 0)$ and (n, n) equals to

$$R_{nn} = \frac{2\sqrt{Rr}}{\pi} \sum_{k=1}^n \frac{1}{2k-1};$$

this formula can be used in your solution. By how much will change the effective resistance between the nodes $(0, 0)$ and $(1, 1)$ when the nodes (n, n) and $(n + 1, n + 1)$ are connected with a piece of wire of negligibly small resistance? In other words, determine $R'_{11} - R_{11}$, where R'_{11} is the new effective resistance between the nodes $(0, 0)$ and $(1, 1)$ after short-circuiting the nodes (n, n) and $(n + 1, n + 1)$. Assume that $n > 1$.

Hint 1 (17th Mar. 2019). There are two ways of solving this problem: (a) using an equivalent 4-port circuit made of 6 resistors; (b) making use of the superposition principle — you need to apply it twice. Mathematically, approach (b) is simpler. With (a), the complexity of the algebra depends on the choice of the equivalent circuit (similarly to Δ and Y -connections for 3-port circuits, different circuits can be used).

Hint 2 (24th Mar. 2019). When using approach (a), note that an equivalent circuit needs to have 6 resistors in generic case (this can be proved similarly to how it is shown that a delta or Y -connection can substitute any 3-terminal circuit consisting of resistors). In order to avoid bridge connections, it is convenient to take a circuit with four resistors along the sides of a square $ABCD$, and two resistors dangling from the nodes B and C . The four output nodes of this equivalent circuit are: A and D , together with the dangling ends B' and C' .

When using approach (b), first apply the superposition principle to determine the voltage between (n, n) and $(n + 1, n + 1)$ when current is driven through $(0, 0)$ and $(1, 1)$. Next, notice that connecting nodes (n, n) and $(n + 1, n + 1)$ with a wire when the nodes (n, n) and $(n + 1, n + 1)$ are connected to a current source is equivalent to drawing a certain unknown current through the nodes (n, n) and $(n + 1, n + 1)$.

By the end of the second week of the second problem, there were 402 registered participants from 54 countries; among them there were 201 high school students, and 201 university students. During the two weeks, in total 21 solutions of the fourth problem were submitted, out of which 16 were correct. For the university students, there is still a chance of getting the speed bonus!

Correct solutions submitted by 17th March 2019:

| Name | country | Uni/PreUni | subm. date/time (GMT) |
|----------------------|-----------|--------------|-----------------------|
| Johanes Suhardjo | Indonesia | HKUST | 10 Mar. 2019 15:42 |
| Felix Christensen | UK | Oxford | 10 Mar. 2019 19:54 |
| Stefan Dolteanu | Romania | PreUni | 10 Mar. 2019 20:55 |
| Thomas Foster | UK | Oxford | 11 Mar. 2019 10:33 |
| Ionel-Emilian Chiosa | Romania | PreUni | 11 Mar. 2019 12:40 |
| Siddharth Tiwary | India | IIT Bombay | 11 Mar. 2019 14:34 |
| Tùng Trần Xuân | Vietnam | PreUni | 11 Mar. 2019 19:52 |
| Vladislav Polyakov | Russia | PreUni | 12 Mar. 2019 06:41 |
| Oliwier Urbański | Poland | PreUni | 12 Mar. 2019 14:34 |
| Eduard Burlacu | Romania | PreUni | 13 Mar. 2019 16:52 |
| Péter Elek | Hungary | PreUni | 13 Mar. 2019 17:41 |
| Mateusz Kapusta | Poland | PreUni | 13 Mar. 2019 22:49 |
| Oliver Lindström | Sweden | PreUni | 18 Mar. 2019 13:35 |
| Morteza Mudrick | Indonesia | PreUni | 20 Mar. 2019 12:09 |
| Ivander J.M. Waskito | Indonesia | PreUni | 20 Mar. 2019 13:59 |
| Batuhan Keskin | Turkey | Bogazici Uni | 13 Mar. 2019 22:49 |